

# Lab – Designing a Circuit from Start to Finish

## Objectives

### Part 1: Use a breadboard to design a circuit in Tinkercad

- Create an account
- Create a new Electronics Lab
- Add components to the breadboard
- Modify the circuit

## Background / Scenario

Tinkercad provides access to virtual electronics, allowing users to design, prototype, and print 3D designs and completed circuits. This activity will guide students through the process of building a custom circuit board.


## Required Resources

- PC with Internet Access
- Tinkercad account (Free)

## Part 1: Use a breadboard to design a circuit in Autodesk 123D Lab View

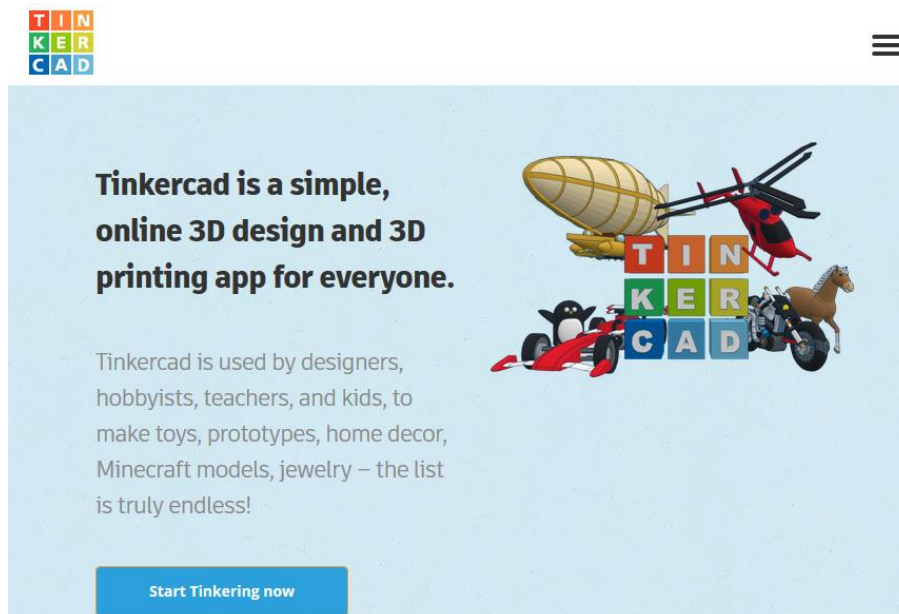
### Step 1: Create an account.

Navigate to <https://www.tinkercad.com/> and sign up for a free account.




### Step 2: Create a new Electronics Lab.

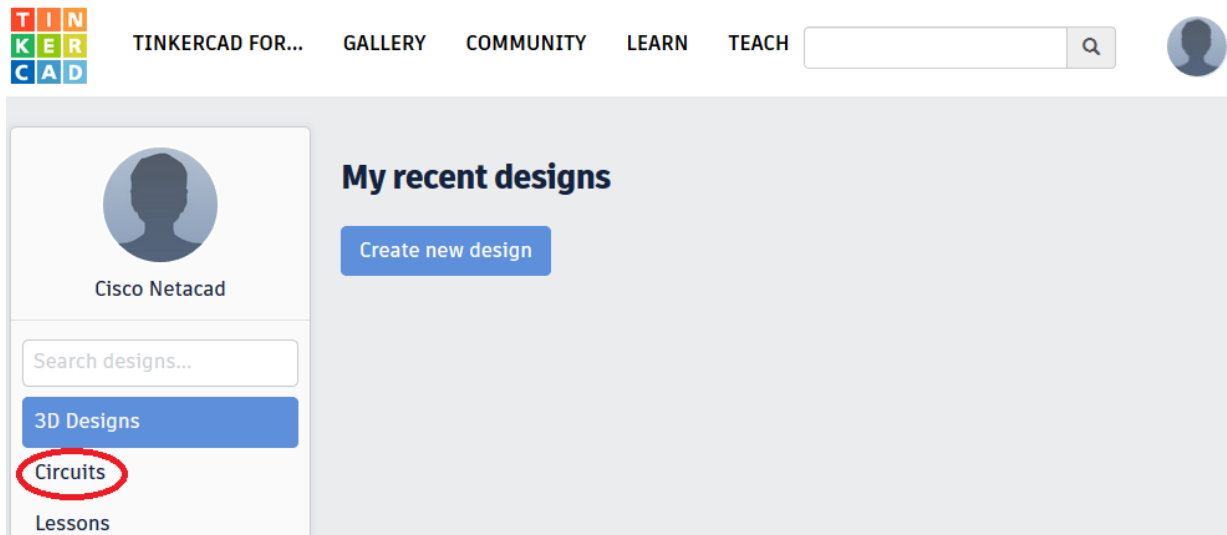- a. Click the link **Circuits** on the left side.




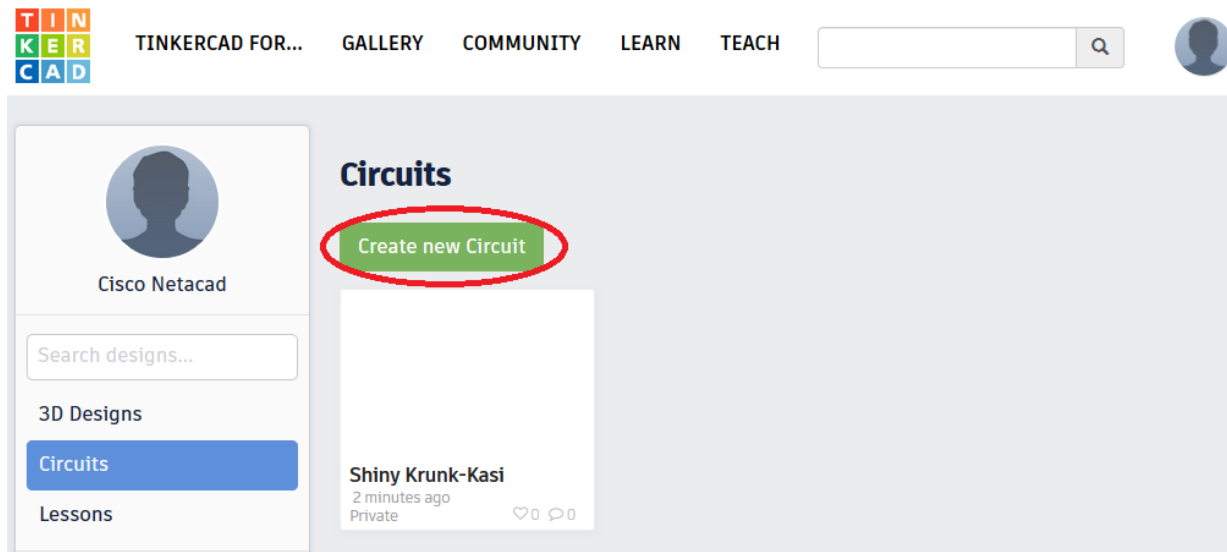- b. Choose the option **Create new Circuit** in the middle of the page.




## Lab – Designing a Circuit from Start to Finish

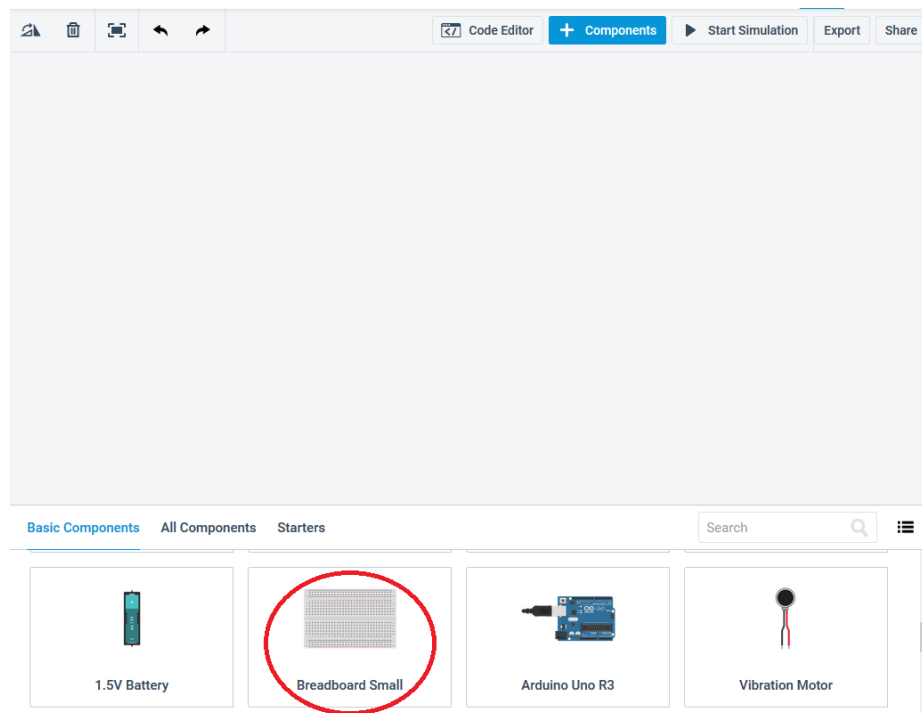- c. Select the component **Breadboard small** from the menu below and click in the whitespace.




Step 3: Add components to the breadboard.

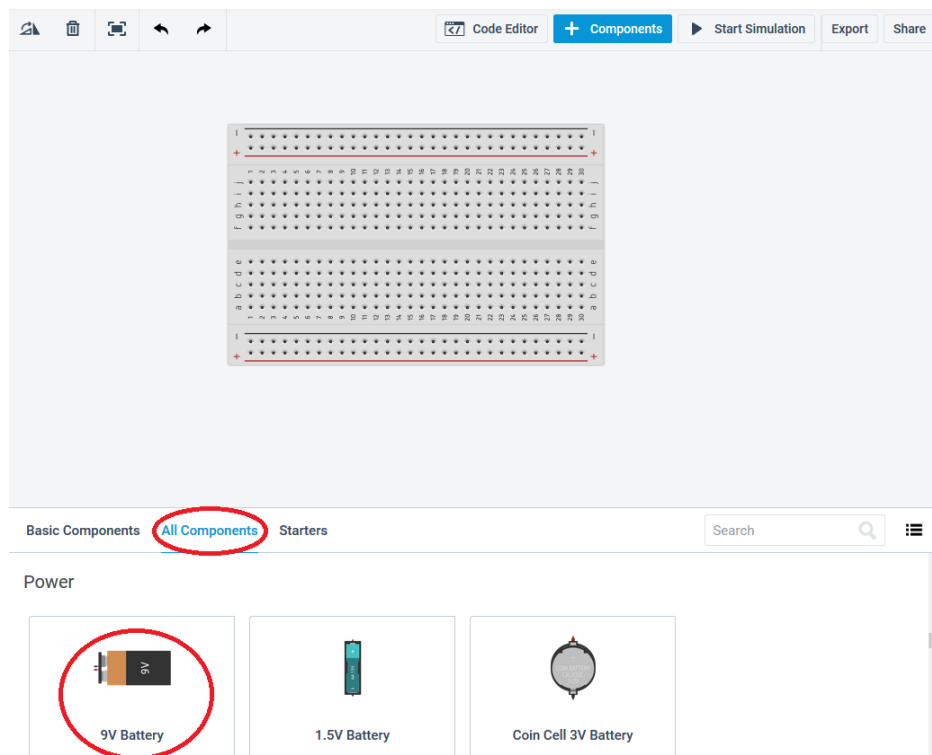- a. Select **All Components** at the bottom of the screen and choose the **9V Battery** in the components list.




## Lab – Designing a Circuit from Start to Finish

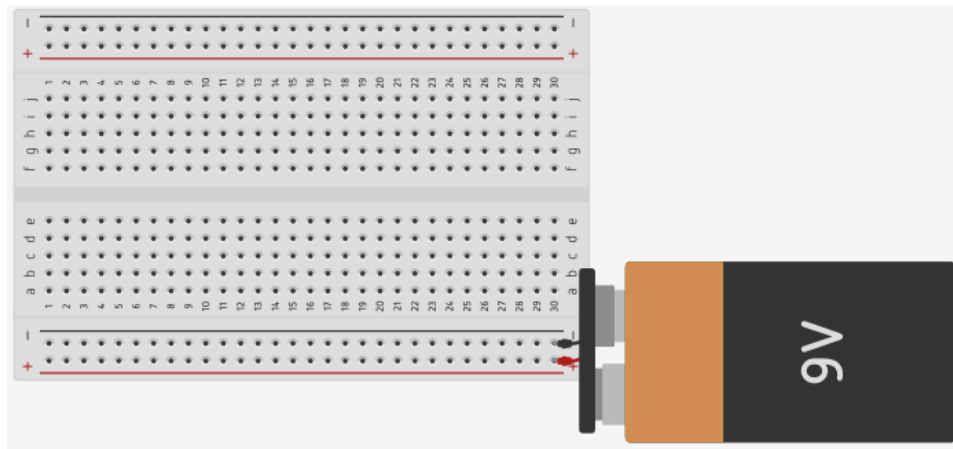- b. Place its terminals on the positive (+) and negative (-) rows at the bottom of the breadboard.




**Note:** Use the scroll wheel on the mouse to zoom in and out.

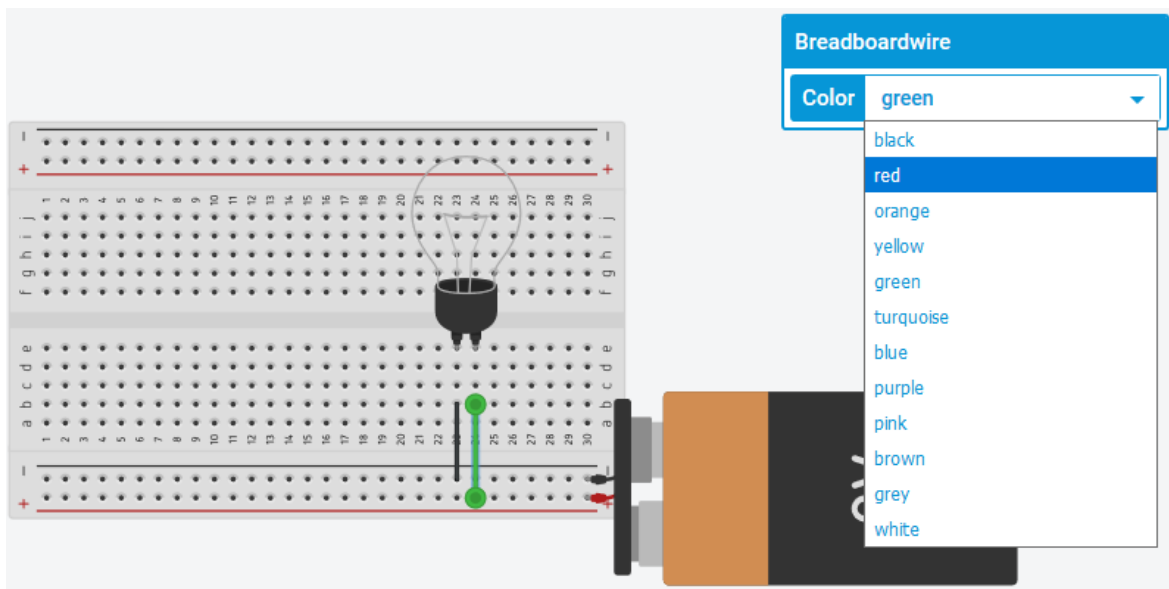- c. Select the **Light Bulb** from the components list and add it to the breadboard.
- d. Draw two wires on the breadboard directly below the light bulb terminals by clicking once on the hole to start of the wire and then click a second time on the hole to end the wire. Use the **Breadboardwire Color** dropdown to change the wire color, select red for positive and black for negative.




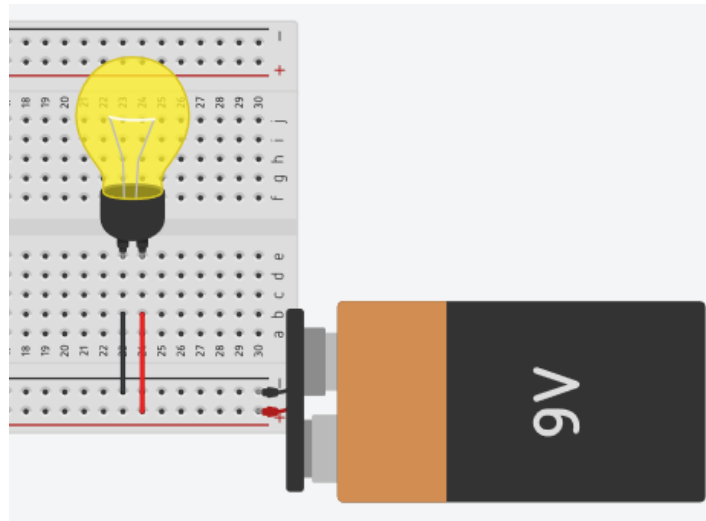- e. Use the **Start Simulation** button to turn on the light.



### Step 4: Modify the circuit.

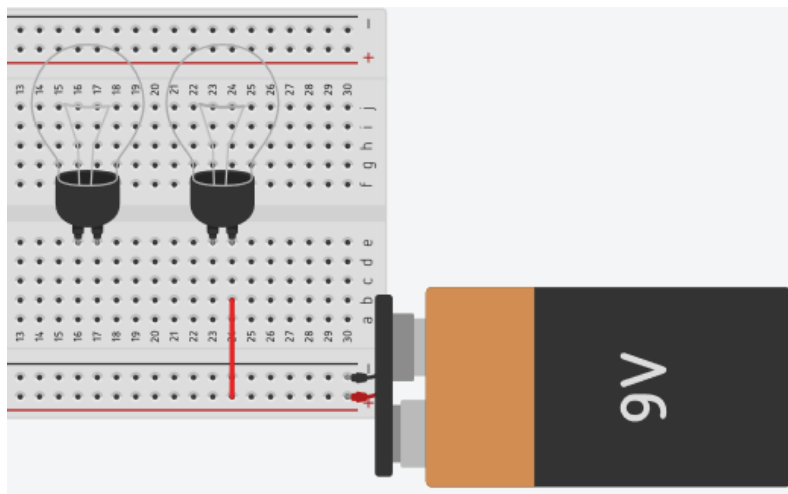
- a. Delete the negative (black) wire from the circuit.
- b. Add a second light on the breadboard.




## Lab – Designing a Circuit from Start to Finish

---

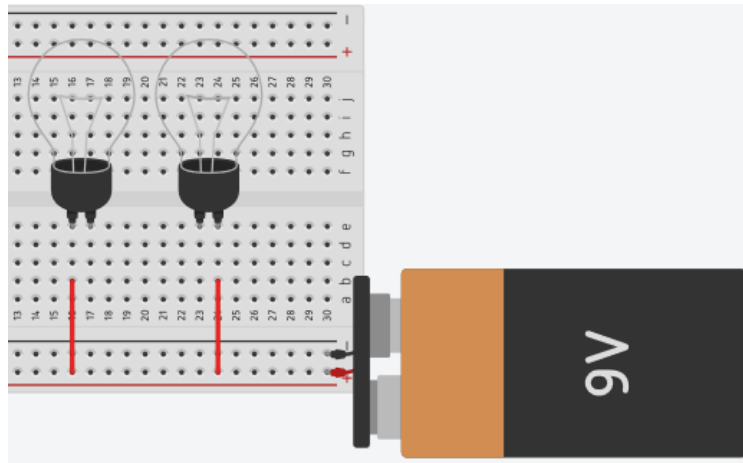- c. Draw a second red wire on the breadboard.




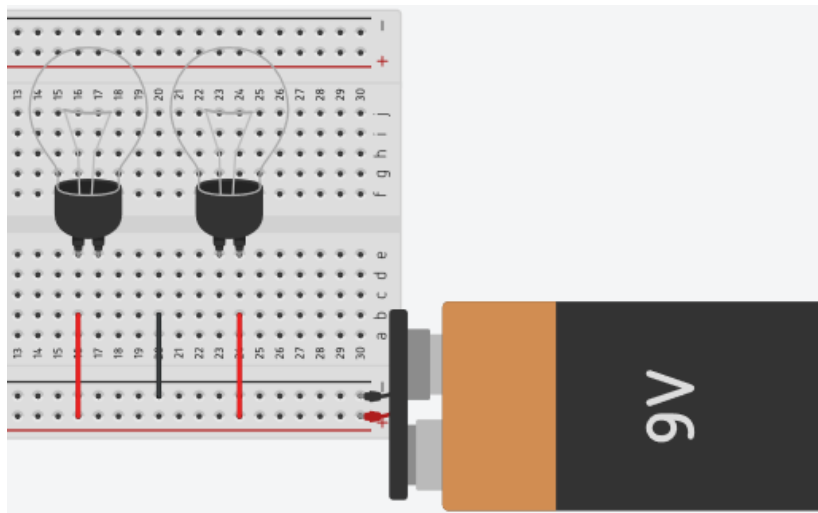- d. Create a new ground wire, negative wire, between the two lights. Color the wire black.




## Lab – Designing a Circuit from Start to Finish

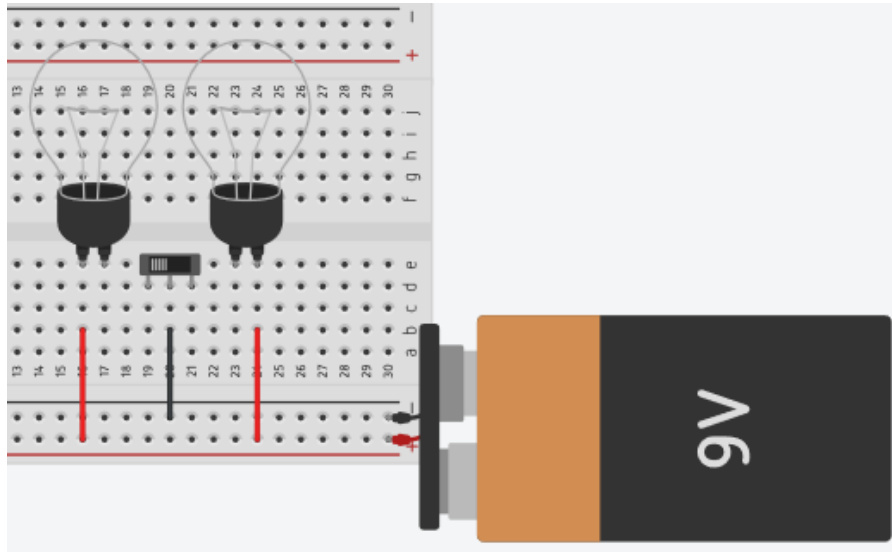- e. Add a **Slideswitch** component to the breadboard drawing, with the center prong in the same column as the black wire.



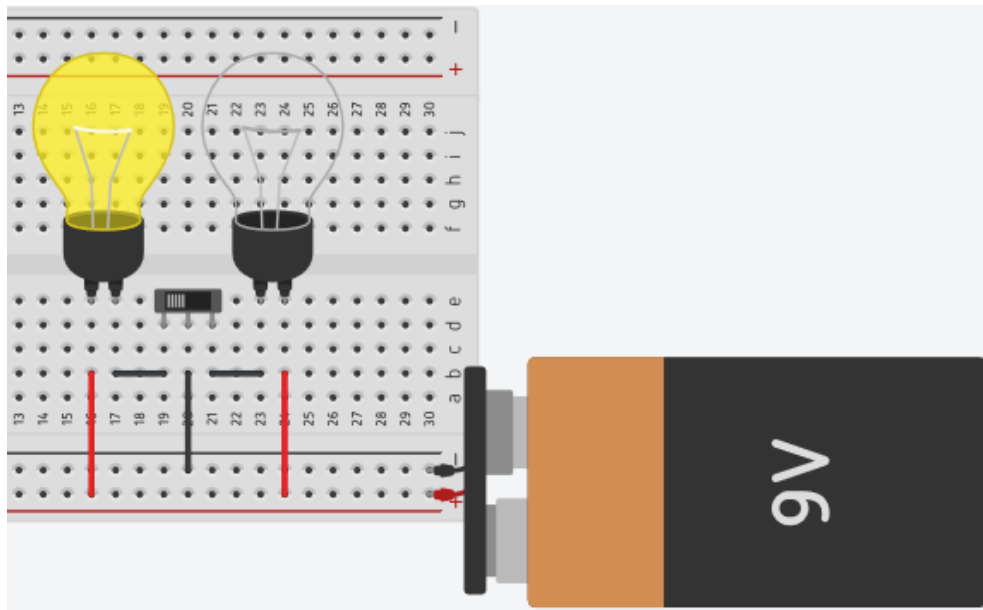- f. Draw wires connecting the slide switch to the columns of the negative terminals for the light bulbs.



- g. Use the **Start Simulation** button and toggle the **Slideswitch** by clicking on it. The switch should complete only one circuit at a time, turning each light on and off individually.

## Reflection

What would happen if a potentiometer replaced the slide switch in the drawing?

---

---